

Lab 3: Sequential Circuit Design

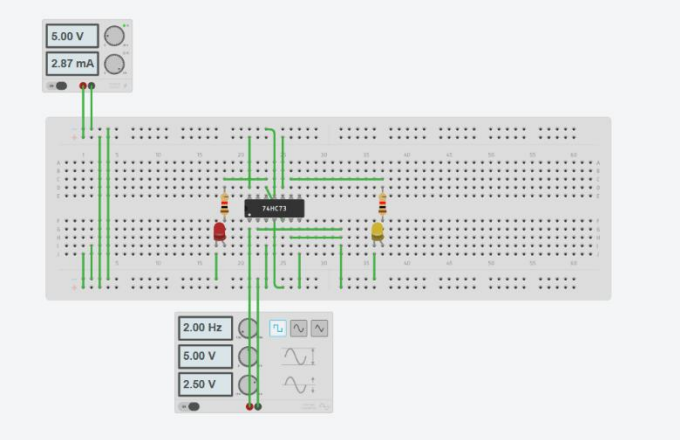2-bit flip-flop counter by using JK flip flop.




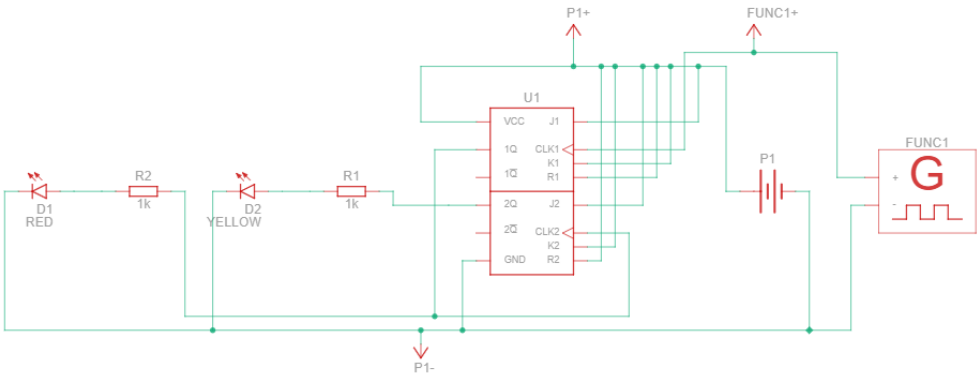


When start the simulation, the LEDs will cycle through binary numbers:

Clock Pulse	**Bit 1 (2Q)**	**Bit 0 (1Q)**	**Decimal Value**
Initial	Off (0)	Off (0)	0
1st Pulse	Off (0)	**On (1)**	1
2nd Pulse	**On (1)**	Off (0)	2
3rd Pulse	**On (1)**	**On (1)**	3
4th Pulse	Off (0)	Off (0)	0 (Resets)


Initial

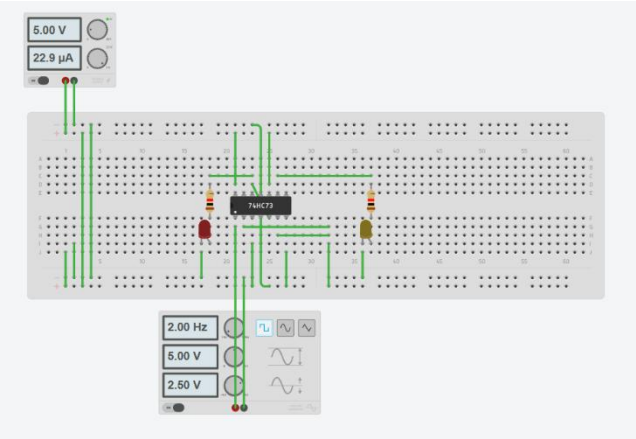


First Pulse

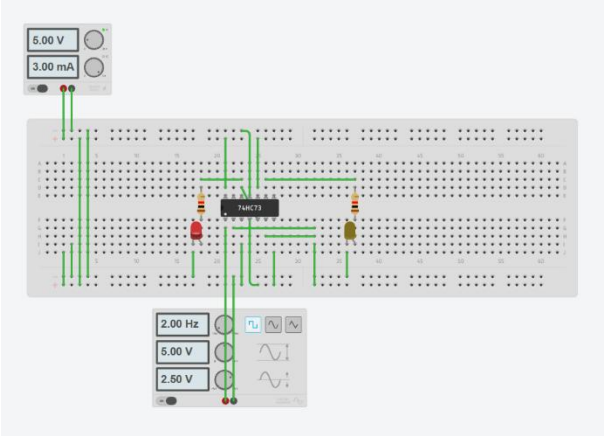

Second Pulse

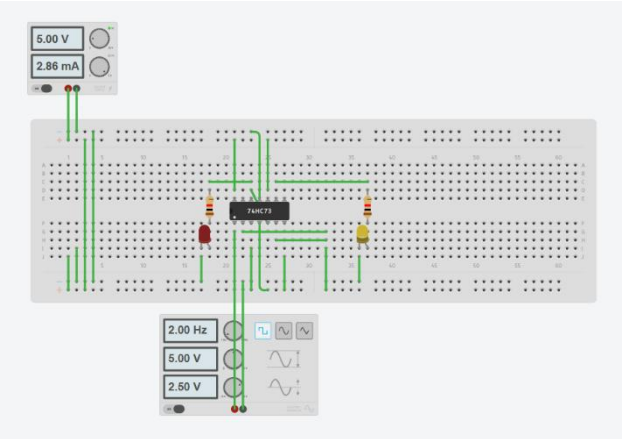


Third Pulse

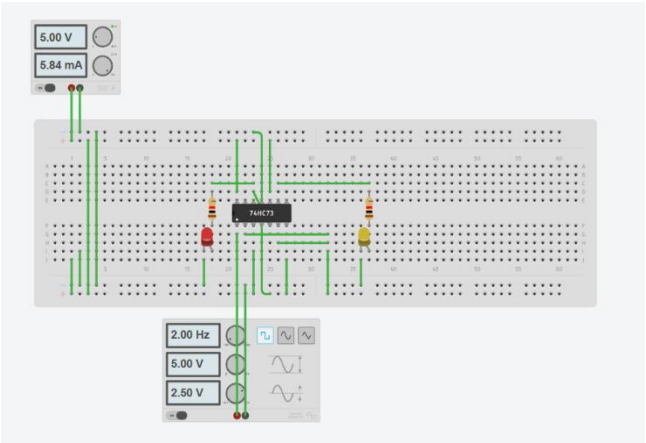


Lab Practices:

1. D flip flop

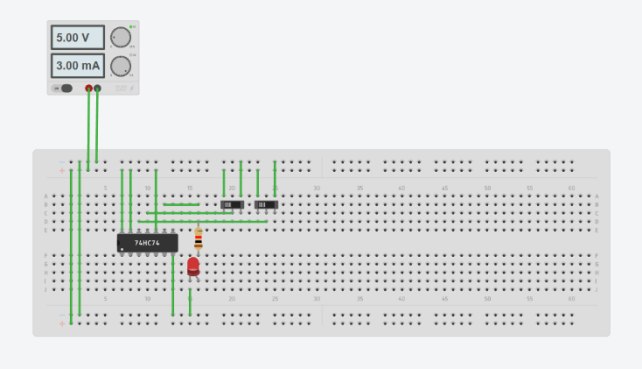

2. J-K flip flop

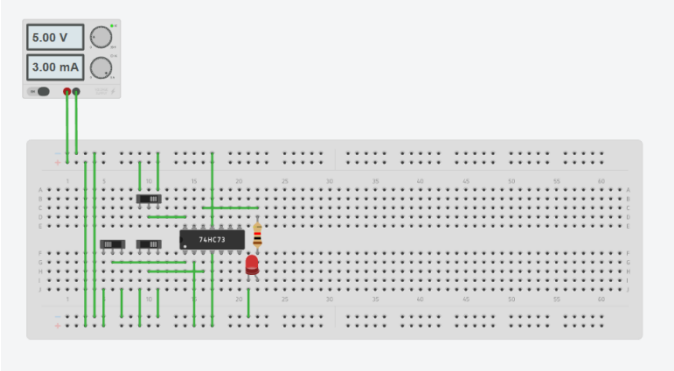

3. 4-bit Lash

