
CSO Lab 7 : Displaying with 8051

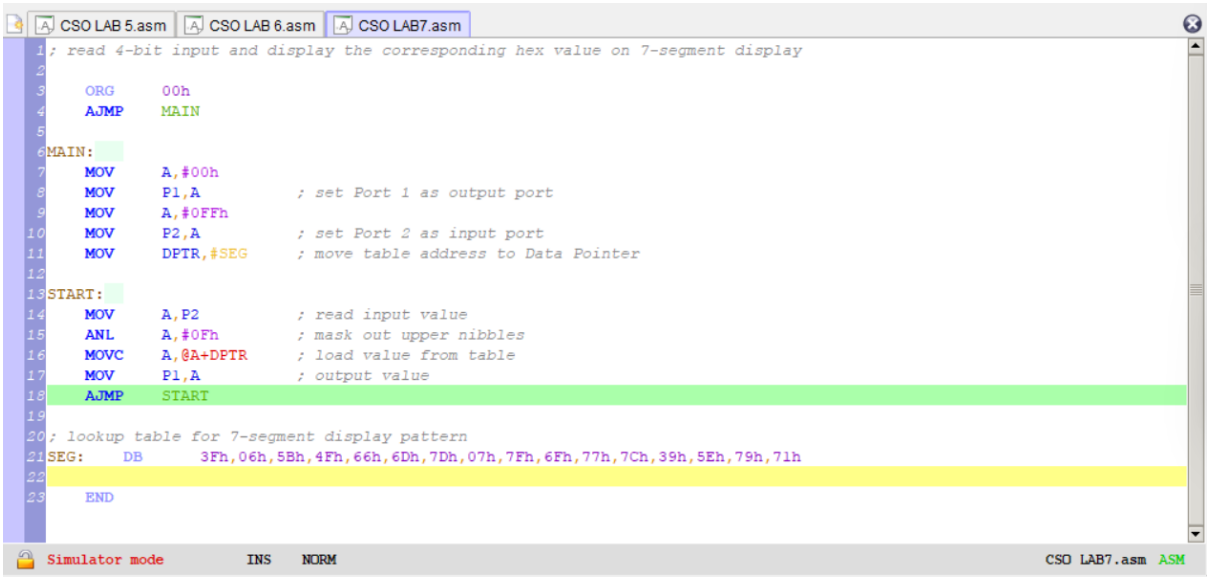Question: Write a program that uses a push button to start and stop a 4-bit binary up counter.



Component	State	Logic Level	Result
Switch	Open	1	Pin is High (VCC)
Switch	Closed	0	Pin is Low (GND)
7-Segment (CA)	Pin Low	0	Segment lights up (Path to GND)
7-Segment (CA)	Pin High	1	Segment is dark (No voltage difference)

Demo Video

https://drive.google.com/drive/folders/1rnfQfxfr03Xsfzd2DmIeLebdBVp3SIGy